

1 RC Circuits

In this problem, we will be using differential equations to find the voltage across a capacitor over time in an RC circuit. We set up our problem by first defining three functions over time: $I(t)$ is the current at time t , $V(t)$ is the voltage across the circuit at time t , and $V_C(t)$ is the voltage across the capacitor at time t .

Recall from 16A that the voltage across a resistor is defined as $V_R = RI_R$ where I_R is the current across the resistor. Also, recall that the voltage across a capacitor is defined as $V_C = \frac{Q}{C}$ where Q is the charge across the capacitor.

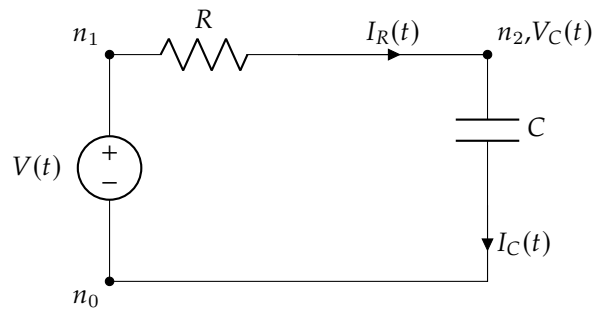


Figure 1: Example Circuit

- a) First, find an equation that relates the current through the capacitor $I_C(t)$ with the voltage across the capacitor $V_C(t)$.

Answer

Charge $Q_C(t)$ and current $I_C(t)$ are related as

$$I_C(t) = \frac{d}{dt} Q_C(t)$$

Differentiating $V_C(t) = \frac{Q_C(t)}{C}$ in terms of t , we get

$$\frac{dV_C(t)}{dt} = \frac{dQ_C(t)}{dt} \frac{1}{C}$$

Using the charge-current relationship above, we can write

$$\frac{d}{dt} V_C(t) = I(t) \frac{1}{C}$$

- b) Using nodal analysis, write a differential equation for the capacitor voltage $V_C(t)$. Note that this is also the voltage for the node n_2 .

Answer

We first list out our device equations to obtain the branch currents for the circuit in Figure 1. The current flowing through the resistor R is given by Ohm's law to be

$$I_R(t) = \frac{V_{n_1}(t) - V_{n_2}(t)}{R}. \quad (1)$$

The current through the capacitor is given by

$$I_C(t) = C \frac{d}{dt} V_{n_2}(t). \quad (2)$$

Next, we write Kirchhoff's current law equations at the nodes. For node n_2 , we have

$$I_R(t) = I_C(t)$$

With n_0 as the reference node, we have

$$V_{n_1} = V(t)$$

. Substituting the values of $I_R(t)$ and $I_C(t)$ from equations 1 and 2 above, we get

$$\begin{aligned} C \frac{d}{dt} V_{n_2}(t) &= \frac{V_{n_1}(t) - V_{n_2}(t)}{R} \\ RC \frac{d}{dt} V_{n_2}(t) &= V(t) - V_{n_2}(t) \end{aligned}$$

Since the node voltage $V_{n_2}(t)$ is same as the capacitor voltage $V_C(t)$, we can express the evolution of capacitor voltage $V_C(t)$ as

$$RC \frac{d}{dt} V_C(t) = V(t) - V_C(t)$$

- c) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_C(0) = V_{DD}$). Let's also assume that $V(t) = 0$ for all $t \geq 0$.

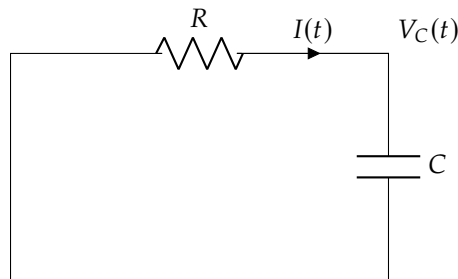


Figure 2: Circuit for part (d)

Solve the differential equation for $V_C(t)$ for $t \geq 0$.

Answer

Because $V(t) = 0$, our differential equation simplifies to

$$RC \frac{dV_C(t)}{dt} + V_C(t) = 0$$

Doing some algebraic manipulations gives us

$$\frac{dV_C(t)}{dt} = -\frac{1}{RC}V_C(t)$$

This equation tells us that we are looking for some function $V_C(t)$ such that when we take its derivative, we get the same function $V_C(t)$ multiplied by a scalar $-\frac{1}{RC}$. Because the derivative is equal to a scalar times itself, we think that the solution $V_C(t)$ will probably be of the form Ae^{bt} , where A and b are both constants. In this case we see that $b = -\frac{1}{RC}$, and we find that

$$V_C(t) = Ae^{-\frac{1}{RC}t}$$

We still need to solve for the constant A in front of the exponential, and we use $V_C(0) = K$ to help us find A . Setting $t = 0$ in the equation gives us

$$\begin{aligned} V_C(0) &= Ae^{-\frac{1}{RC}0} \\ &= Ae^0 \\ &= A \\ &= V_{DD} \end{aligned}$$

Thus, we see that $A = V_{DD}$, and our solution is

$$V_C(t) = V_{DD}e^{-\frac{1}{RC}t}$$

- d) Now, let's suppose that we start with an uncharged capacitor $V_C(0) = 0$. We apply some constant voltage $V(t) = V_{DD}$ across the circuit. Solve the differential equation for $V_C(t)$ for $t \geq 0$.

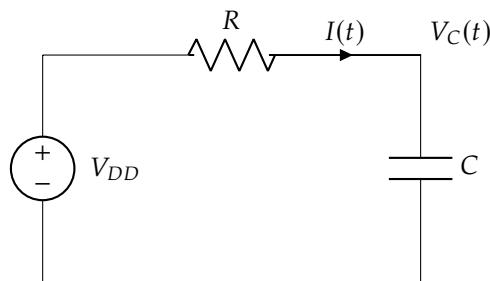


Figure 3: Circuit for part (e)

Answer

Substituting $V(t) = V_{DD}$ into our solution from part (c):

$$RC \frac{dV_C(t)}{dt} + V_C(t) = V_{DD}$$

Rearranging the differential equation we get

$$\frac{d}{dt}V_C = -\frac{1}{RC}V_C(t) + \frac{V_{DD}}{RC}$$

This differential equation looks similar to the one in the previous part but we notice that there is an extra $\frac{V_{DD}}{RC}$ term. If we were to again guess the solution $V_C(t) = Ae^{-\frac{1}{RC}t}$ we see that:

$$\begin{aligned} -\frac{1}{RC}Ae^{-\frac{1}{RC}t} &= -\frac{1}{RC}Ae^{-\frac{1}{RC}t} + \frac{V_{DD}}{RC} \\ 0 &= \frac{V_{DD}}{RC} \end{aligned}$$

We end up with an equation that is impossible to solve meaning there must have been a problem with our guess. Therefore, we will improve our guess by trying the solution $V_C(t) = Ae^{-\frac{1}{RC}t} + B$. Taking its derivative and plugging it into the differential equation, we get

$$\begin{aligned} \frac{dV_C(t)}{dt} &= -\frac{1}{RC}V_C(t) + \frac{V_{DD}}{RC} \\ -\frac{1}{RC}Ae^{-\frac{1}{RC}t} &= -\frac{1}{RC}(Ae^{-\frac{1}{RC}t} + B) + \frac{V_{DD}}{RC} \\ 0 &= -\frac{B}{RC} + \frac{V_{DD}}{RC} \end{aligned}$$

This tells us that $B = V_{DD}$. Now to solve for A , we plug in the initial condition $V_C(0) = 0$

$$V_C(0) = Ae^{-\frac{1}{RC} \cdot 0} + V_{DD} = A + V_{DD} = 0$$

It follows that $A = -V_{DD}$ so our final solution to the differential equation will be

$$V_C(t) = -V_{DD}e^{-\frac{1}{RC}t} + V_{DD} = V_{DD}(1 - e^{-\frac{1}{RC}t})$$

Alternate Method using Substitution of Variables:

We want to arrange this equation to be in a form that we know how to solve:

$$\frac{d}{dt}V_C = \frac{V_{DD} - V_C(t)}{RC}$$

This is not quite the form we have seen before, as the term on the right is not equal to the term being differentiated. Let's instead define a new variable $\tilde{V}_C(t) = V_C(t) - V_{DD}$. Note that $\frac{d\tilde{V}_C(t)}{dt} = \frac{dV_C(t)}{dt}$. We can substitute these into our differential equation and obtain

$$\begin{aligned} RC \frac{dV_C(t)}{dt} + V_C(t) - V_{DD} &= 0 \\ RC \frac{d\tilde{V}_C(t)}{dt} + \tilde{V}_C(t) &= 0 \end{aligned}$$

In this equation, we have now removed V_{DD} from the left hand because of how we defined $\tilde{V}_C(t)$. We can now solve the differential equation using the same method as in the previous part to get

$$\tilde{V}_C(t) = Ae^{-\frac{t}{RC}}$$

Substituting $V_C(t) = V_{DD} + \tilde{V}_C(t)$ back into this equation gives us

$$V_C(t) = V_{DD} + Ae^{-\frac{t}{RC}}$$

Using in the initial condition $V_C(0) = 0$, we get:

$$0 = V_{DD} + Ae^{-\frac{0}{RC}} = V_{DD} + A \implies A = -V_{DD}$$

Therefore,

$$\begin{aligned} V_C(t) &= V_{DD} - V_{DD}e^{-\frac{t}{RC}} \\ &= V_{DD}(1 - e^{-\frac{t}{RC}}) \end{aligned}$$

2 Graphing RC Responses

Consider the following RC Circuit with a single resistor R , capacitor C , and voltage source $V(t)$.

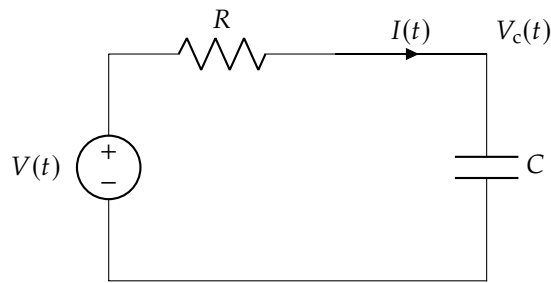


Figure 4: Example Circuit

- a) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_c(0) = V_{DD}$) and that $V(t) = 0$ for all $t \geq 0$. Plot the response $V_c(t)$.

Answer


We can represent the RC Circuit with the following first order differential equation

$$\frac{dV_c(t)}{dt} = -\frac{1}{RC}V_c(t)$$

Since the initial condition is $V_c(0) = V_{DD}$, the solution to this differential equation will be $V_c(t) = V_{DD}e^{-\frac{t}{RC}}$.

To plot this response by using a graphing tool or by plotting points and connecting the dots. We've plotted the response when $V_{DD} = 5$ and $RC = 1$.

Voltage Graph for Discharging Capacitor

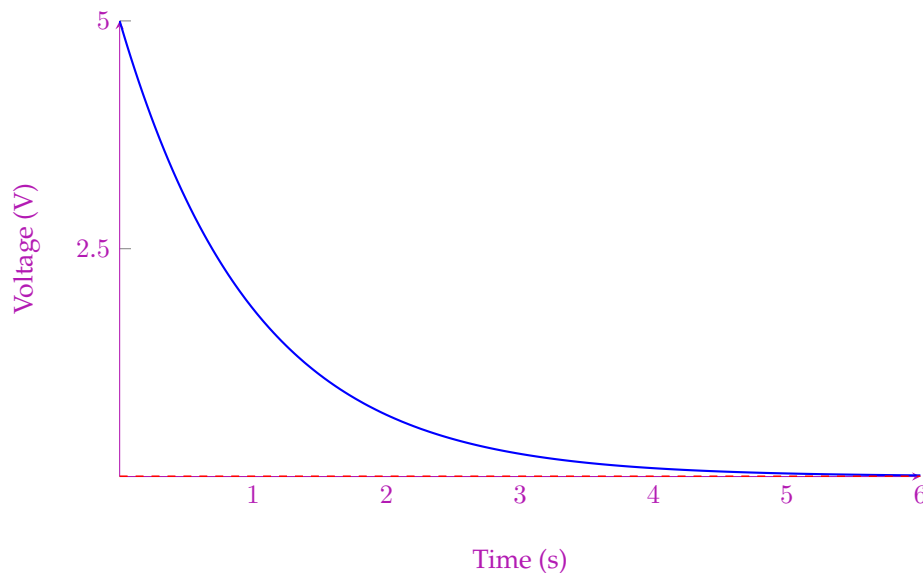


- b) Now let's suppose that at $t = 0$, the capacitor is uncharged ($V_c(0) = 0$) and that $V(t) = V_{DD}$ for all $t \geq 0$. Plot the response $V_c(t)$.

Answer

We can represent the RC Circuit with the following first order differential equation

$$\frac{dV_c(t)}{dt} = -\frac{1}{RC}V_c(t) + \frac{V_{DD}}{RC}$$

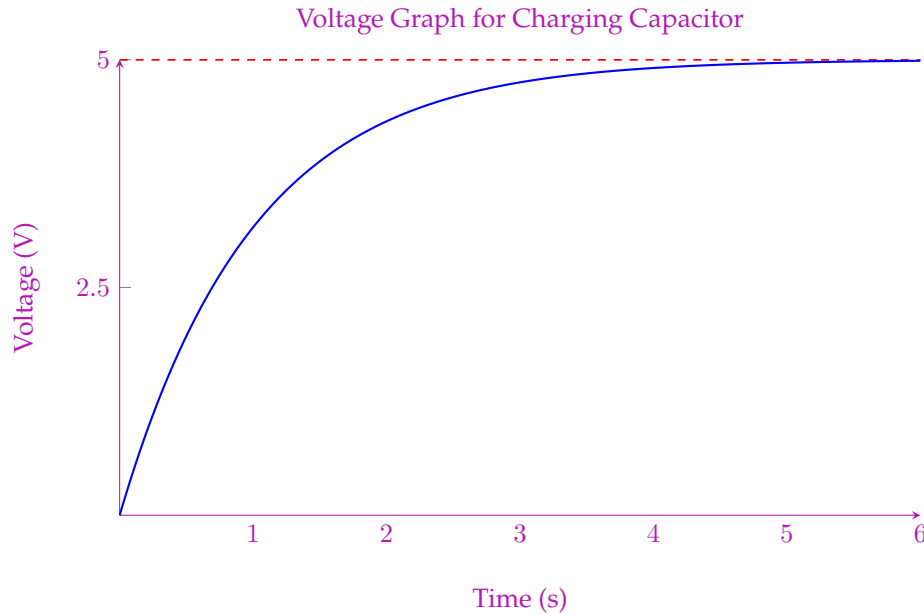The solution to this differential equation is $V_c(t) = V_{DD}(1 - e^{-\frac{t}{RC}})$ and we can plot its response again by using a graphing tool. We've plotted the response when $V_{DD} = 5$ and $RC = 1$.



To better understand our responses, we now define a **time constant** which is a measure of how long it takes for the capacitor to charge or discharge. Mathematically, we define τ as the time at which $V_c(\tau)$ is $\frac{1}{e} = 36.8\%$ away from its steady state value.

- c) Suppose that $V_{DD} = 5\text{ V}$, $R = 100\ \Omega$, and $C = 10\ \mu\text{F}$. What is the time constant τ for this circuit?

Answer

The time constant for an RC circuit with a single resistor and capacitor will be $\tau = RC$. To show this, we look at the discharging case in part (a), let $V_c(\tau) = \frac{V_{DD}}{e}$ and solve for τ .

$$\begin{aligned} V_c(\tau) &= V_{DD}e^{-\frac{\tau}{RC}} = \frac{V_{DD}}{e} \\ e^{-\frac{\tau}{RC}} &= \frac{1}{e} \\ \ln(e^{-\frac{\tau}{RC}}) &= \ln\left(\frac{1}{e}\right) \\ -\frac{\tau}{RC} &= -1 \\ \tau &= RC \end{aligned}$$

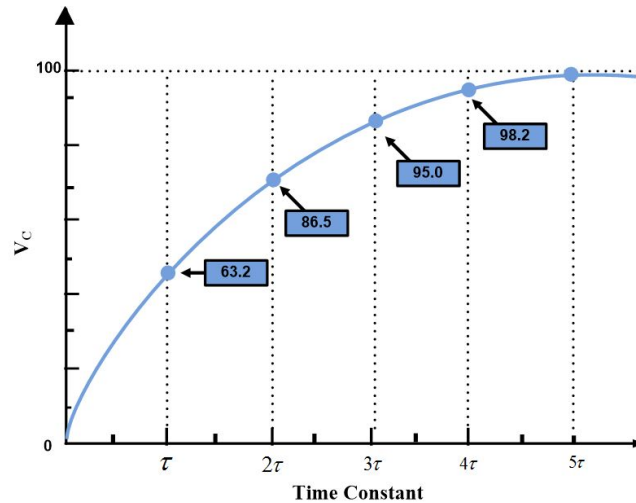


Figure 5: Different values of capacitor voltage at different times, relative to τ .

Alternatively we could've solved for τ by considering the charging case from part (b) and solved for $V_c(\tau) = V_{DD}(1 - \frac{1}{e})$.

- d) Going back to part (b), on what order of magnitude of time (nanoseconds, milliseconds, 10's of seconds, etc.) does this circuit settle (V_c is $> 95\%$ of its value as $t \rightarrow \infty$)?

Answer

The time constant τ of an RC circuit is just $\tau = RC$. For our circuit:

$$\tau = RC = 100\ \Omega \cdot 10\ \mu\text{F} = 0.001\ \text{s}$$

After 3 time constants, the voltage will be 95% of its steady state value

$$3\tau = 0.003\ \text{s}$$

The circuit will settle on the order of milliseconds. Alternatively, this value can be found by using algebra:

$$0.95V_{DD} = V_{DD}(1 - e^{-\frac{t}{RC}})$$

$$-0.05 = -e^{-\frac{t}{RC}}$$

$$0.05 = e^{-\frac{t}{RC}}$$

$$\ln(0.05) = -\frac{t}{RC}$$

$$-3 = -\frac{t}{0.001}$$

$$t = 0.003\ \text{seconds}$$

- e) Give 2 ways to reduce the settling time of the circuit if we are allowed to change one component in the circuit.


Answer

To reduce settling time we reduce τ . We can achieve this by

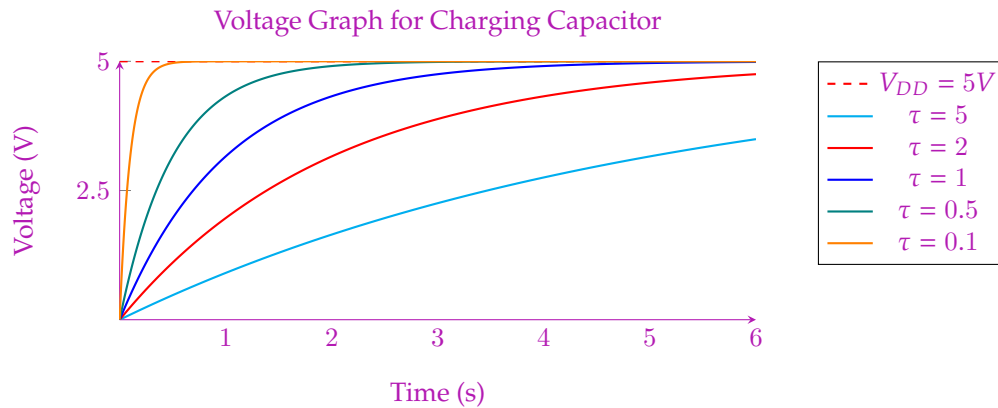
- a) Lowering the value of R or
- b) Lowering the value of C .

Notice how the value of V_{DD} does not change the settling time.


We've plotted the responses for a couple of τ values below. As τ approaches 0, the response V_c will approach an ideal square wave.



- f) Suppose we have a source $V(t)$ that alternates between 0 and $V_{DD} = 1V$. Given $RC = 0.1s$, plot the response V_c if $V_c(0) = 0$.

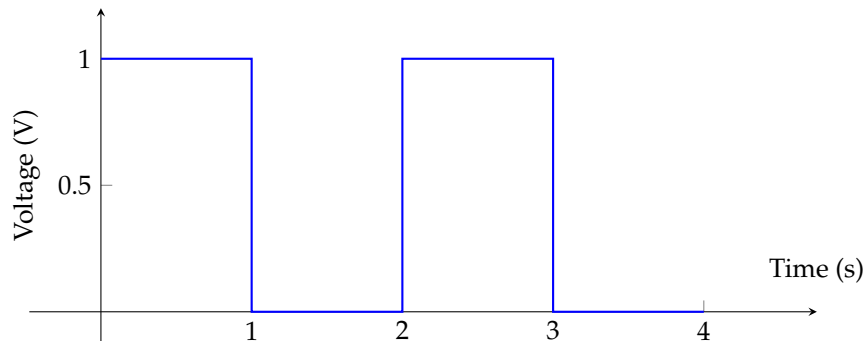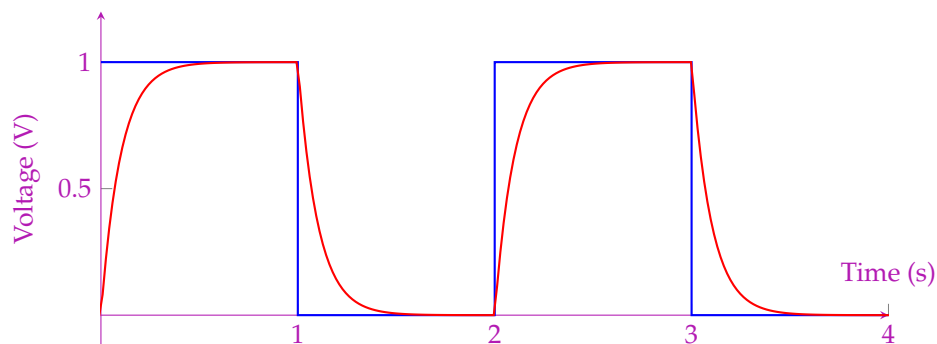**Answer**

The input switches between high and low every second while $\tau = RC = 0.1s$. This means the capacitor will charge and discharge for 10τ so we can approximate it as fully charged and discharged after 1 second.



g) Now suppose we have the same source $V(t)$ but $RC = 1$ s, plot the response V_c if $V_c(0) = 0$.

Answer

The input has stayed the same while $\tau = RC = 1$ s. This means the capacitor will only charge and discharge for one time constant or up to around 63%.

